



第七章 MOS存储器


7.2 MOS存储器单元




MOS存储器单元

- DRAM单元
- SRAM单元
- ROM单元


DRAM单元结构和工作原理

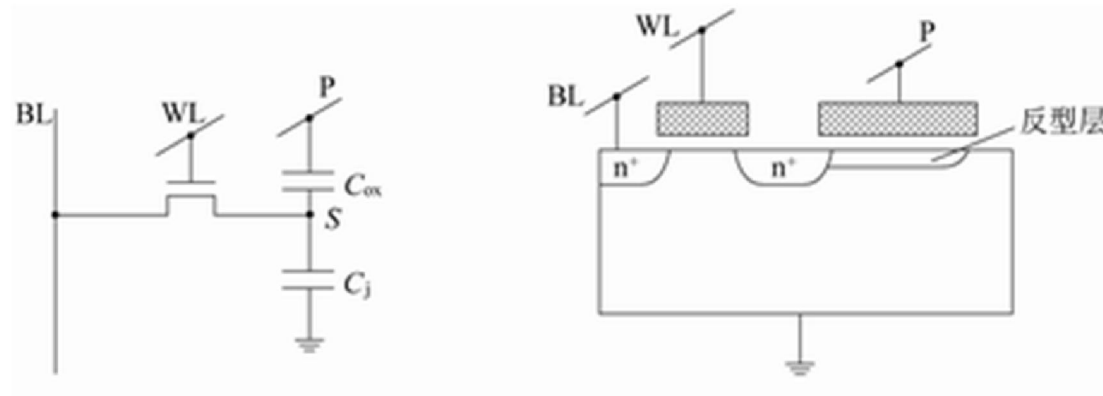

$$\text{存储电容 } C_s = A(C_{ox} + C_j)$$

 


单元存“0”

 


单元存“1”

DRAM单元工作过程

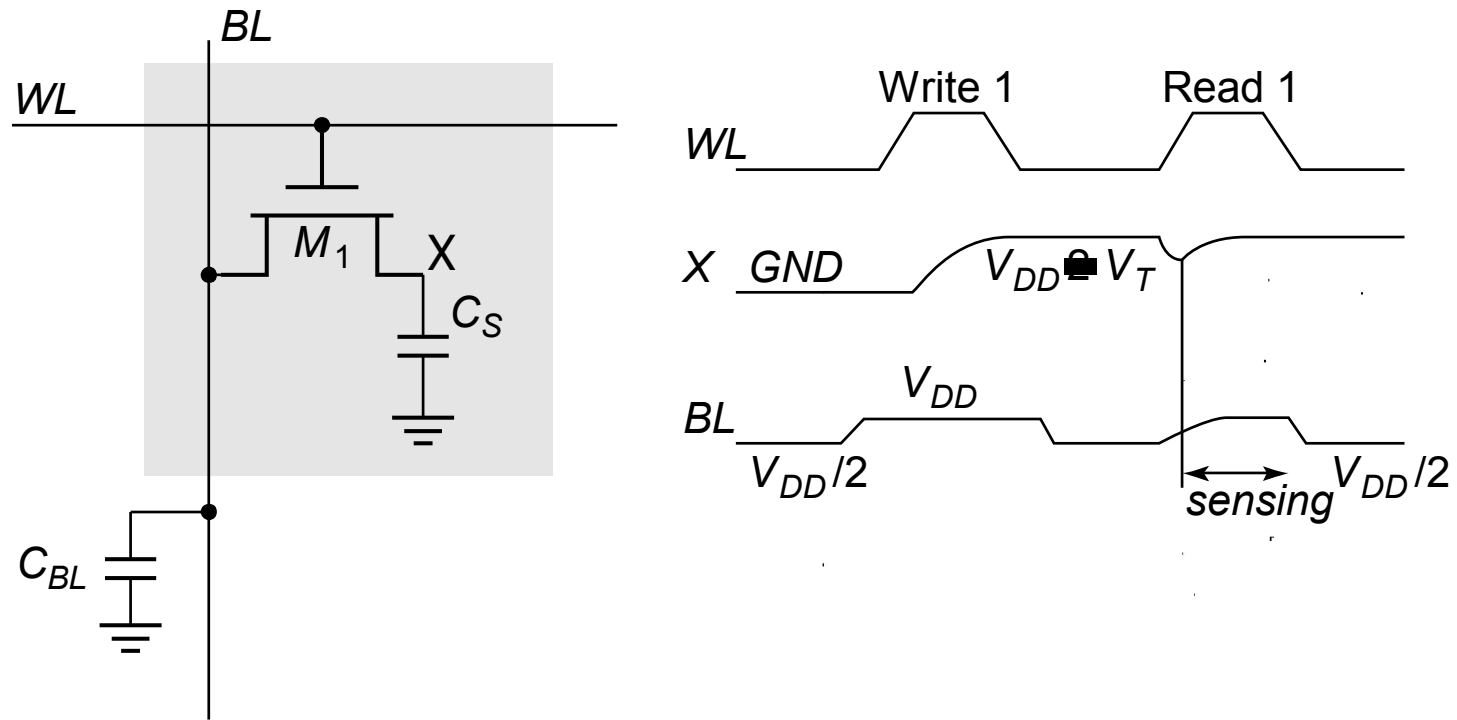

信息的写入

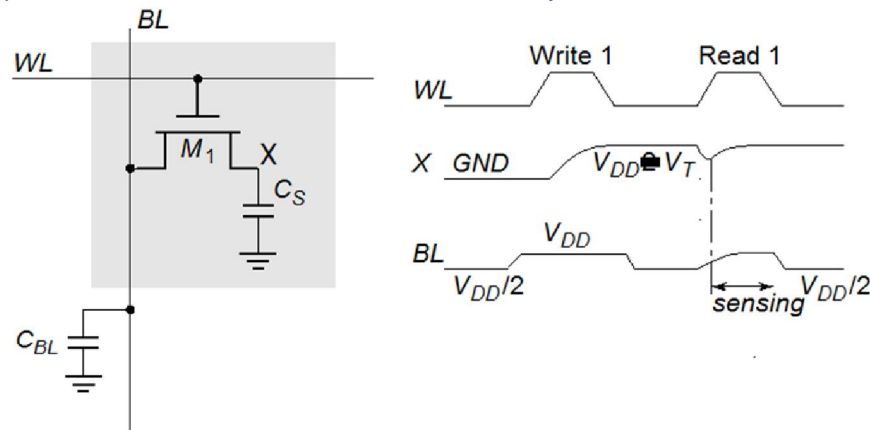

■ 写“1”

预备动作：位线高电平

过程：字线高电平 → 门管导通 → 位线向存储
电容充电

结果：存储节点的高电平： $V_{S1} = V_{DD} - V_{TN}$


■ 写“0”

预备动作：位线低电平

过程：字线高电平 → 门管导通 → 位线对存储
电容放电

结果：存储节点的低电平： $V_{S0} = 0$

信息的读取

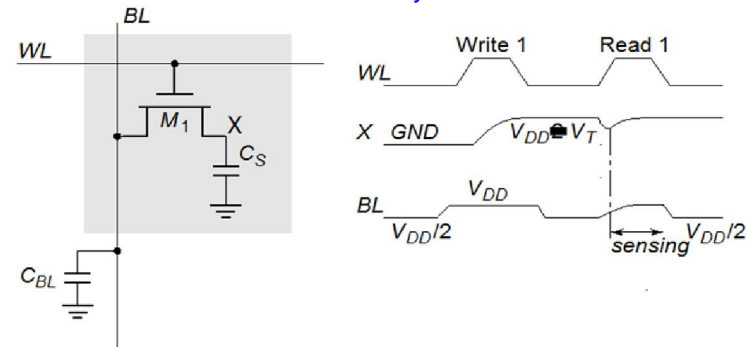

- 预备动作：位线预充电


$$V_R = \frac{V_{S1} + V_{S0}}{2}$$

- 过程：字线高电平-〉 门管导通-〉

存储电容和位线电容发生电荷分享

$$V_{B0} = \frac{V_R C_B + V_{S0} C_S}{C_B + C_S} < V_R$$
 
$$V_{B1} = \frac{V_R C_B + V_{S1} C_S}{C_B + C_S} > V_R$$



$$V_{B0} = \frac{V_R C_B + V_{S0} C_S}{C_B + C_S} < V_R$$

$$V_{B1} = \frac{V_R C_B + V_{S1} C_S}{C_B + C_S} > V_R$$

电荷传输效率

- 为了反映DRAM单元读出特性，引入单元电荷传输效率的参数 T

$$T = \frac{\Delta V_B}{\Delta V_S} = \frac{V_{B1} - V_{B0}}{V_{S1} - V_{S0}} = \frac{1}{1 + C_B/C_S}$$

由于位线电容比存储电容大很多，因此电荷传输效率远小于1




DRAM读操作存在**2**个问题：读出后单元信号被破坏，读出信号微弱

解决办法：设置灵敏再生放大器**(S/R)**




DRAM单元结构

- 性能优值：增加存储单元电容值
- 面积优值：减小单元占用面积
- 利用立体结构在不增加平面面积情况下，增加存储电容
- 利用高K材料增加存储电容
   
$$T = \frac{\Delta V_B}{\Delta V_S} = \frac{V_{B1} - V_{B0}}{V_{S1} - V_{S0}} = \frac{1}{1 + C_B / C_S}$$







DRAM单元结构：沟槽电容

   

Trench Cell

- 垂直方向，向下拓展空间


DRAM单元结构：叠置电容

   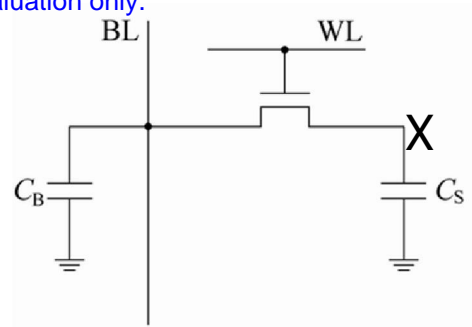

- 垂直方向：向上拓展空间

Stacked-capacitor Cell

DRAM单元结构发展

 




MOS存储器单元

- DRAM单元
- SRAM单元
- ROM单元


SRAM单元结构和工作原理

■ 高阻多晶硅电阻负载的单元

 



问题：功耗与可靠性的矛盾

CMOS单元电路



 


- 解决电阻负载单元中功耗和可靠性的矛盾
- 优势：
 - 只有泄漏电流引起的静态功耗
 - 保证单元存储信息可靠




6-transistor CMOS SRAM Cell

 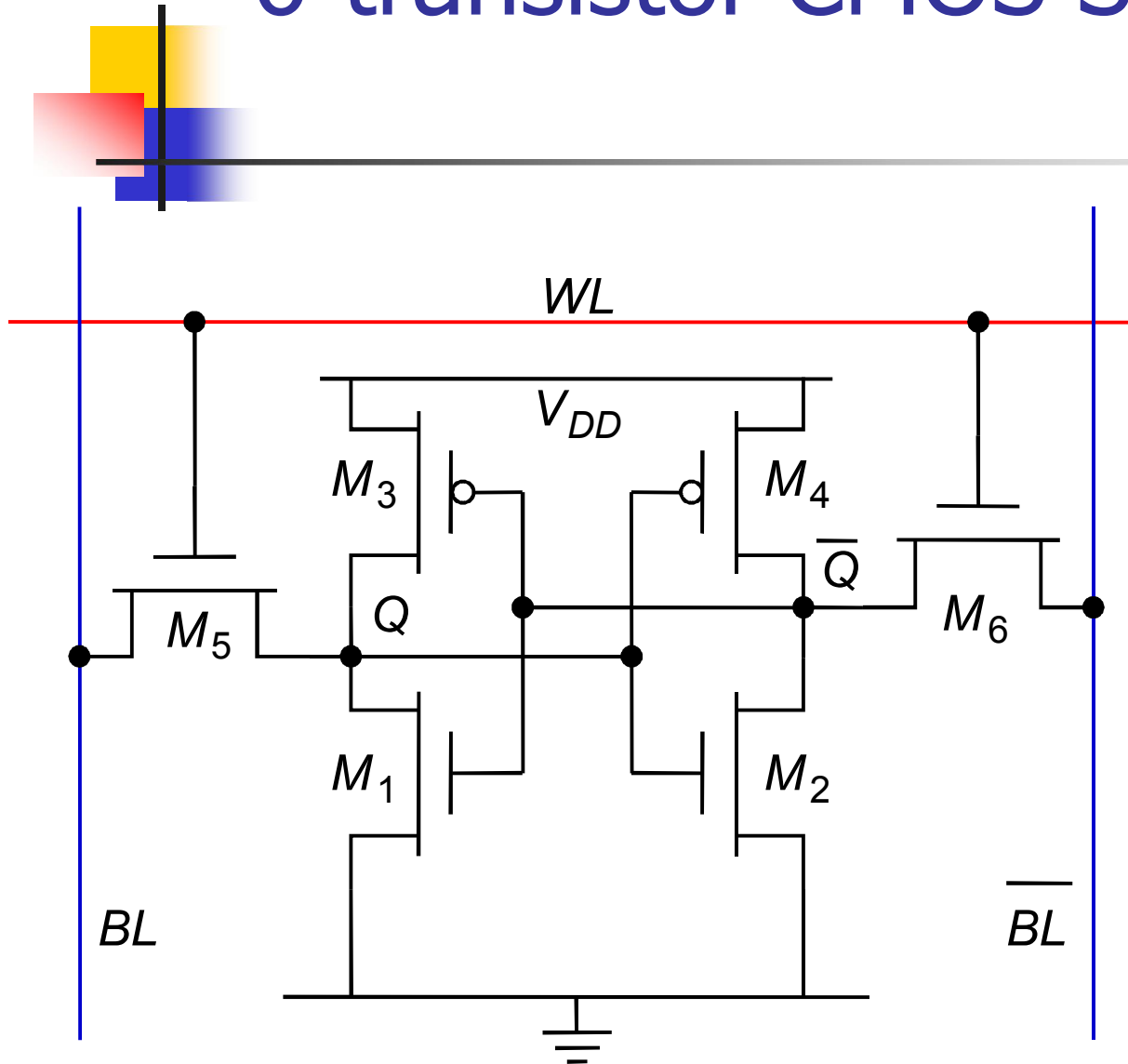


CMOS SRAM 读操作

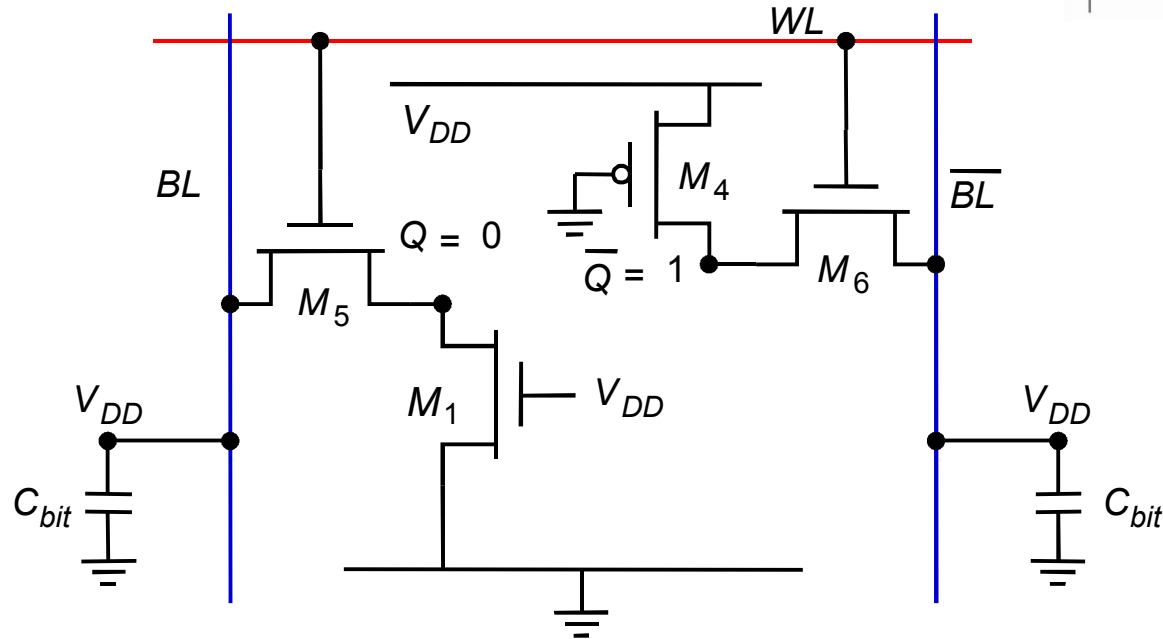  


CMOS SRAM 写操作

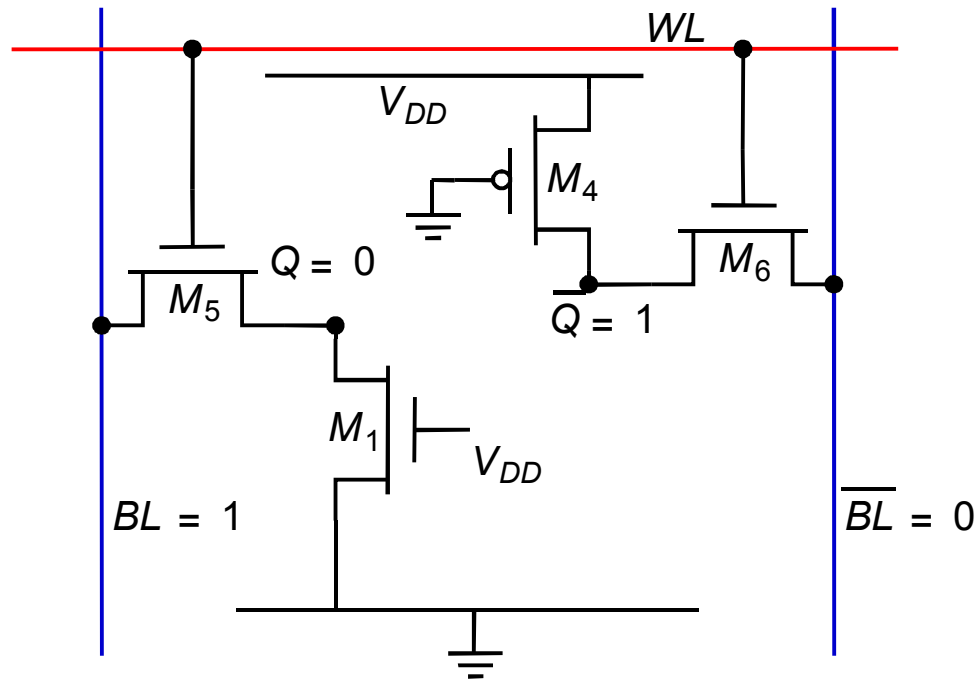  

CMOS单元结构

 

- TFT负载的CMOS单元

 

SRAM Characteristics

Table 12-2 Comparison of CMOS SRAM cells used in 1-Mbit memory
(from [Takada91])







	Complementary CMOS	Resistive Load	TFT Cell
Number of transistors	6	4	4 (+2 TFT)
Cell size	58.2 μm^2 (0.7- μm rule)	40.8 μm^2 (0.7- μm rule)	41.1 μm^2 (0.8- μm rule)
Standby current (per cell)	10^{-15} A	10^{-12} A	10^{-13} A



MOS存储器单元

- DRAM单元
- SRAM单元
- ROM单元

Read-Only Memory Cells

 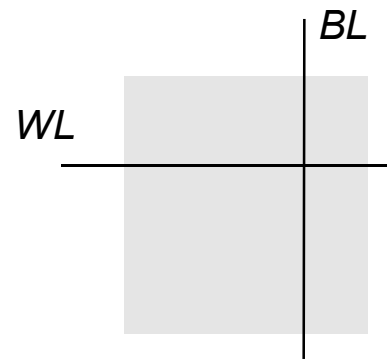    



Diode ROM

MOS ROM 1


MOS ROM 2

掩模编程的ROM单元

  
- 一个**MOS**管构成一个单元
- 用制作**MOS**管的某一次光刻版实现编程：
 - 离子输入，有源区，引线孔




并联结构 ROM

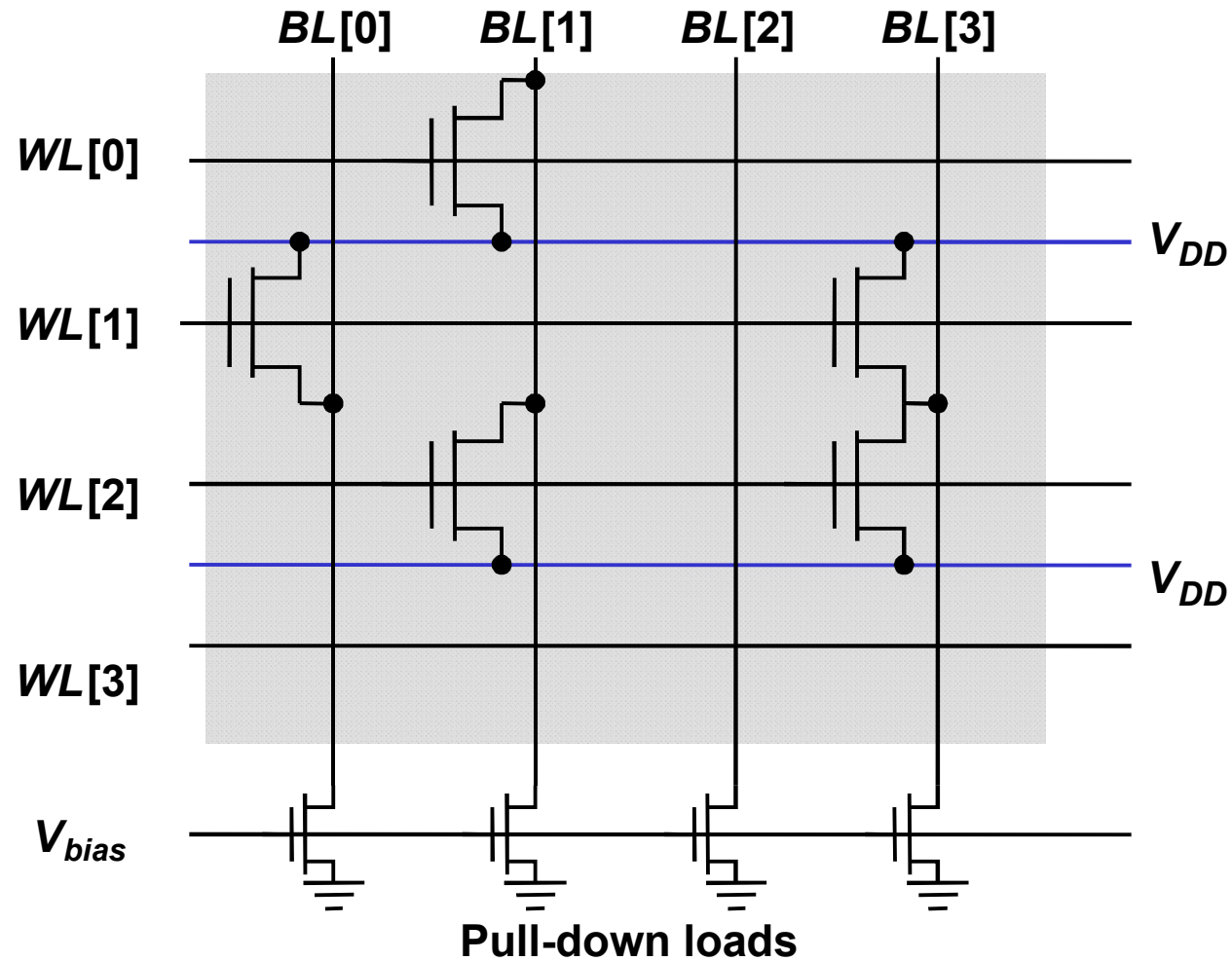


并联结构 ROM

 

并联结构 ROM 版图:接触孔编程

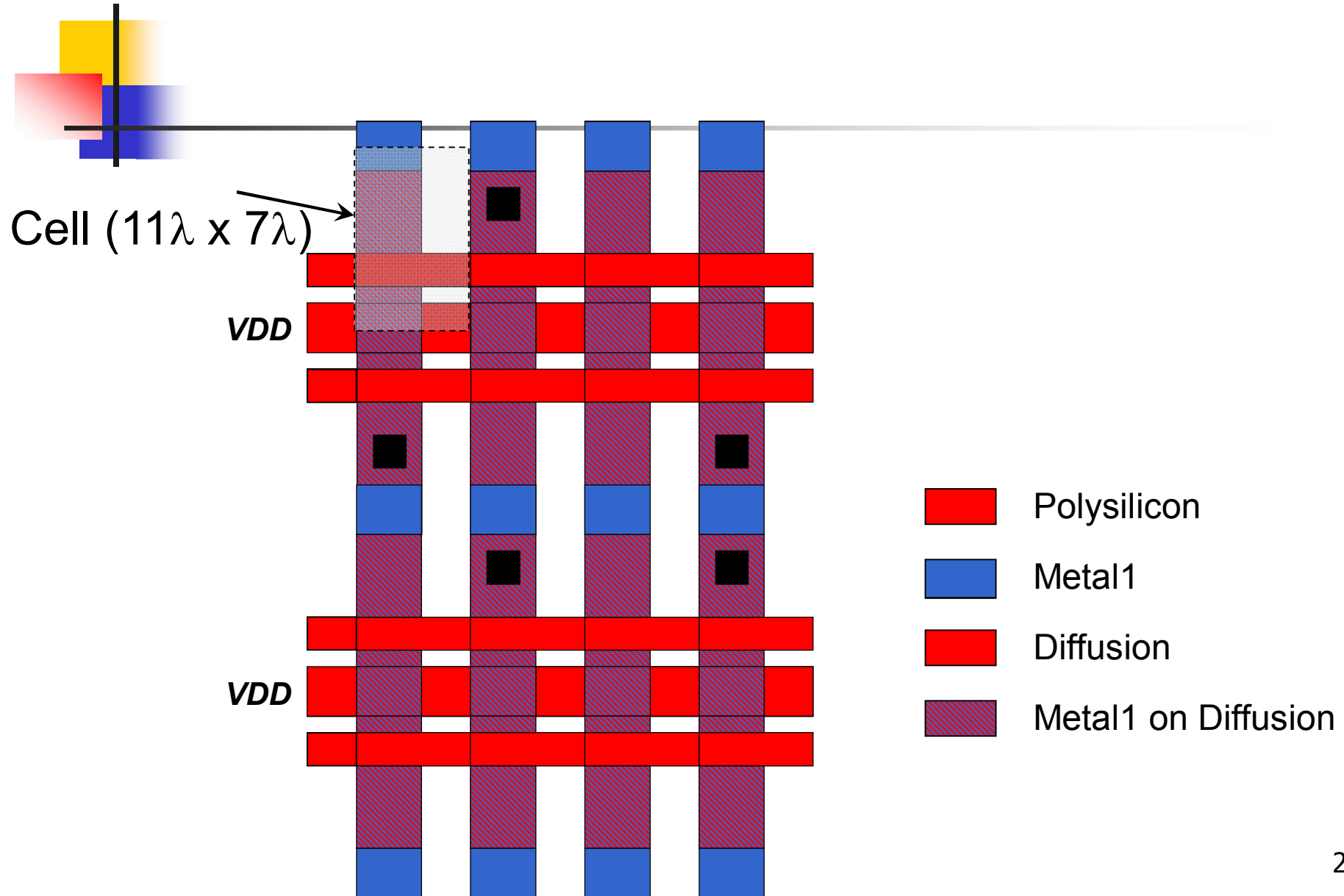


串并联结构 ROM

 


All word lines high by default with exception of selected row
只有选中字线的一行下拉，其他行维持上拉

串并联ROM版图

 




Cell ($5\lambda \times 6\lambda$)


 
No contact to VDD or GND necessary;
drastically reduced cell size
Loss in performance compared to NOR ROM



离子注入编程


-  Polysilicon
-  Threshold-altering implant
-  Metal1 on Diffusion

并联结构ROM等效电路

 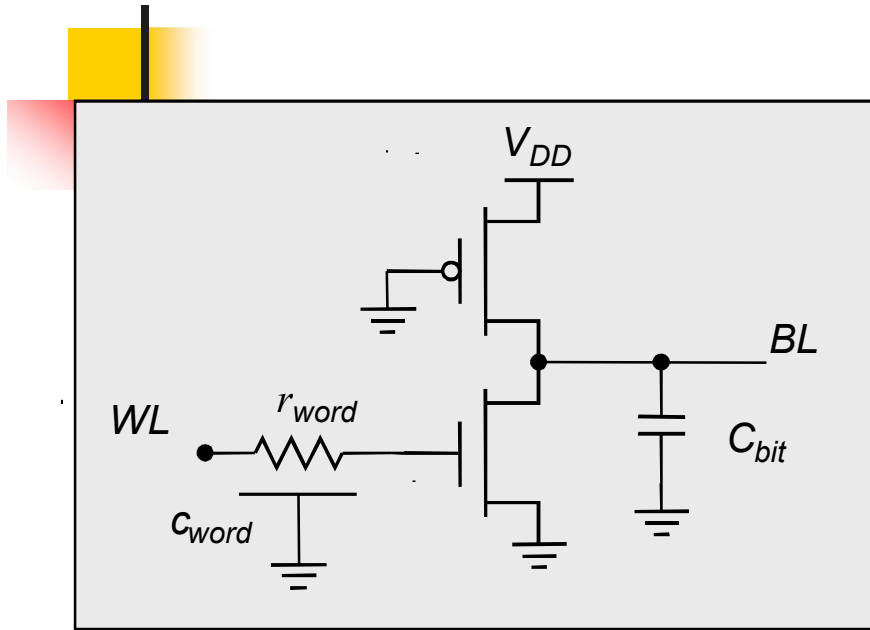


- 字线电容、电阻
 - Wire capacitance and gate capacitance
 - Wire resistance (polysilicon)
- 位线电容电阻
 - Resistance not dominant (metal)
 - Drain capacitance

减小字线延迟

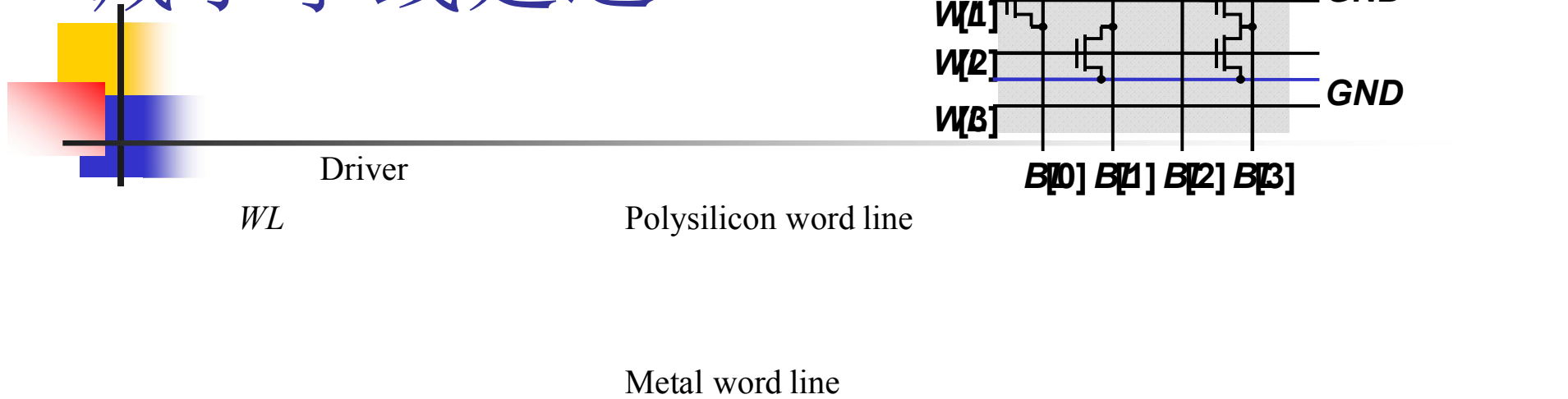

 
(a) Driving the word line from both sides



(b) Using a metal bypass


(c) Use silicides

Precharged MOS ROM

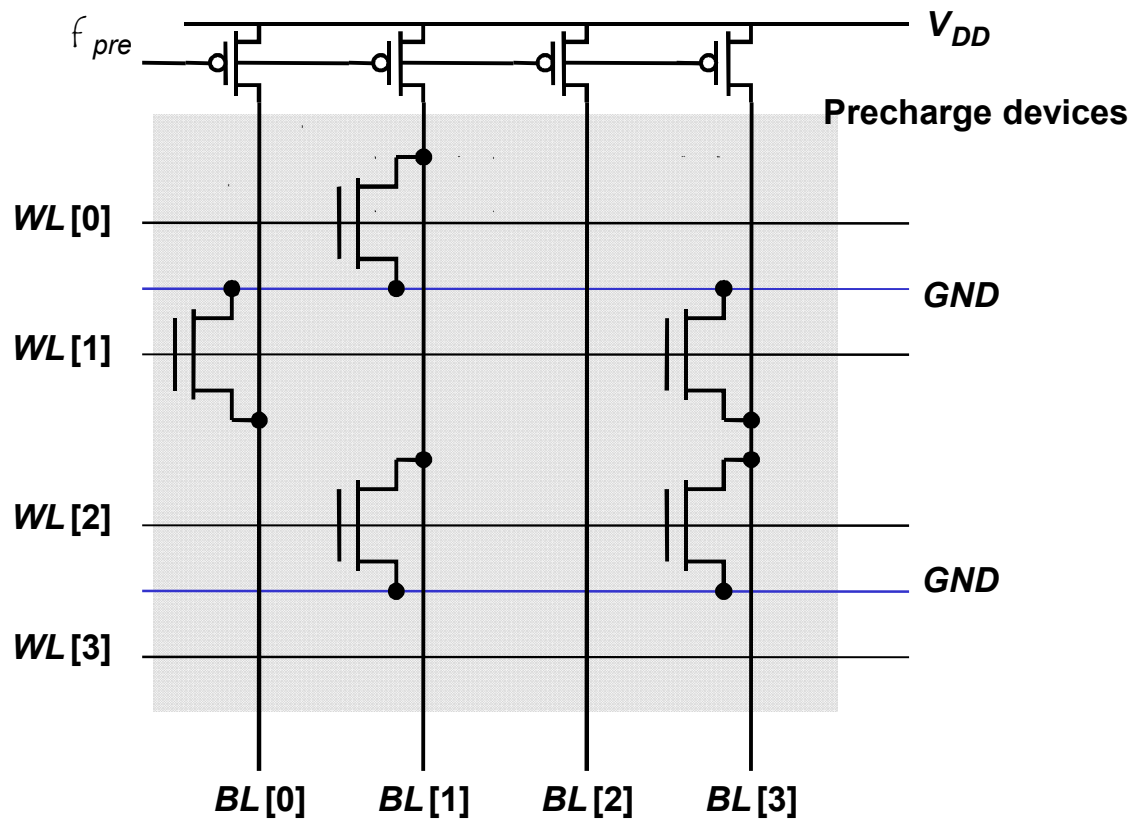

浮栅MOS管构成的EPROM

- 利用浮栅上的存储电荷改变**MOS**管的阈值电压

 


(a) EPROM


(b) EEPROM

(c) Flash

The Floating-gate transistor

 


Device cross-section

 

Schematic symbol

Floating-Gate Transistor Programming




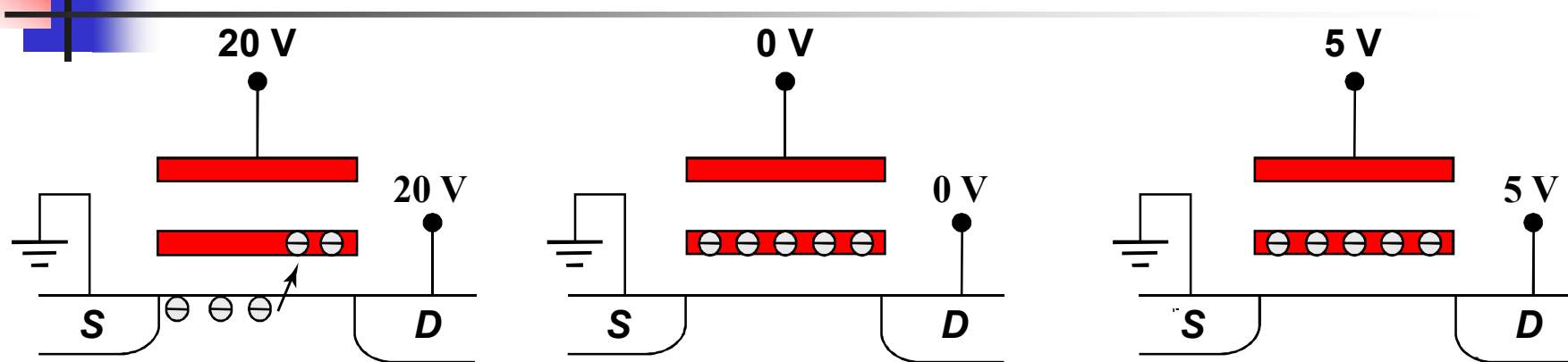


Avalanche injection


Removing programming voltage leaves charge trapped

Programming results in higher V_T .


A "Programmable-Threshold Transistor

  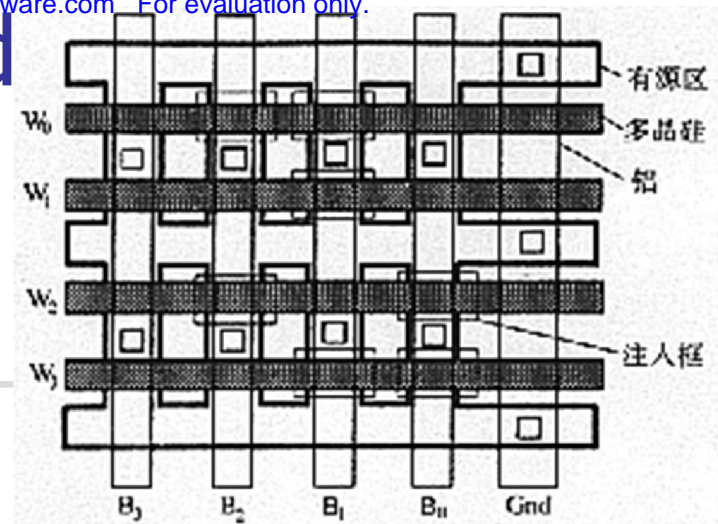 

FLOTOX EEPROM

 


FLOTOX transistor

 





Fowler-Nordheim
I-V characteristic

Flash EEPROM


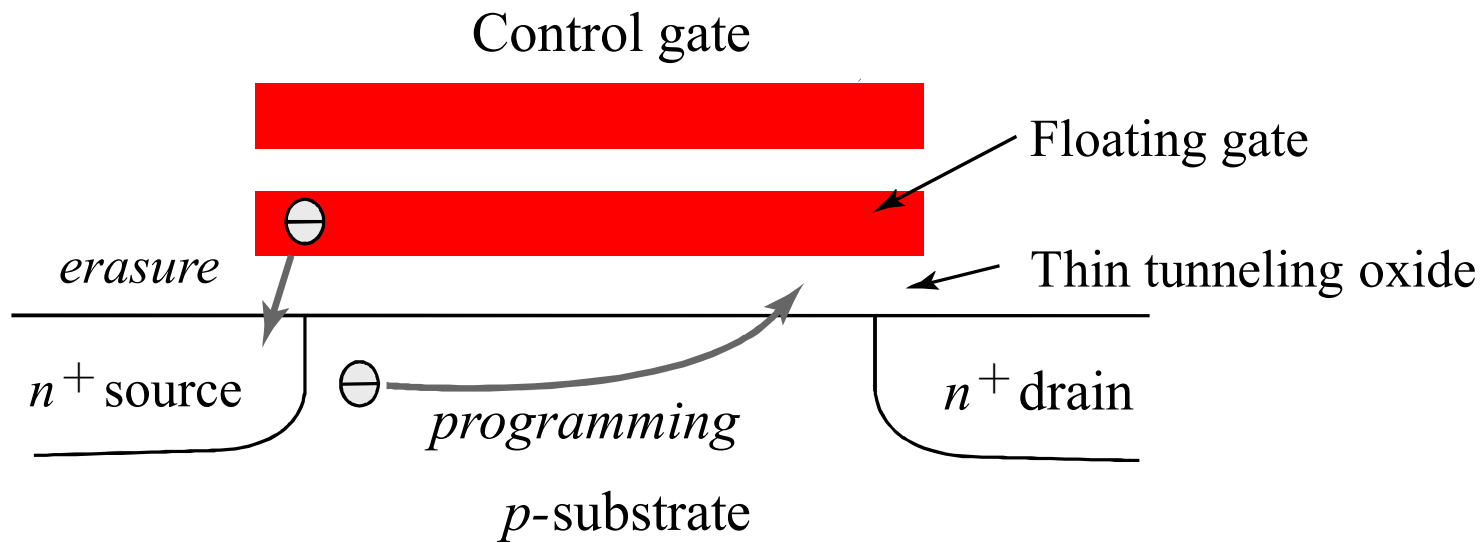


Many other options ...



并联结构 Flash 的擦除过程

  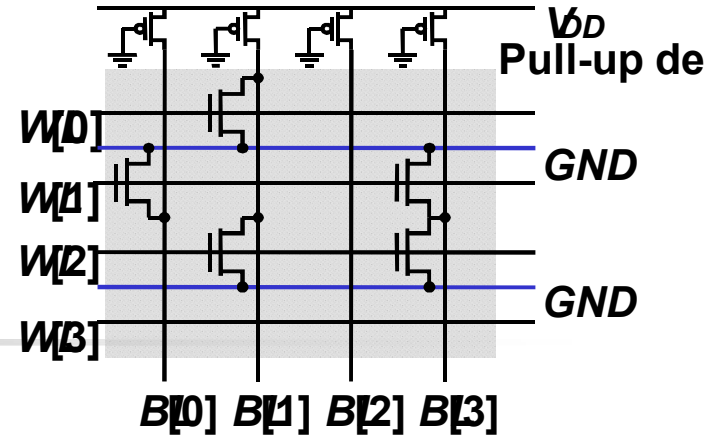 



并联结构 Flash 写入过程

  


并联结构Flash的读出过程

  

串联结构 Flash Memory

 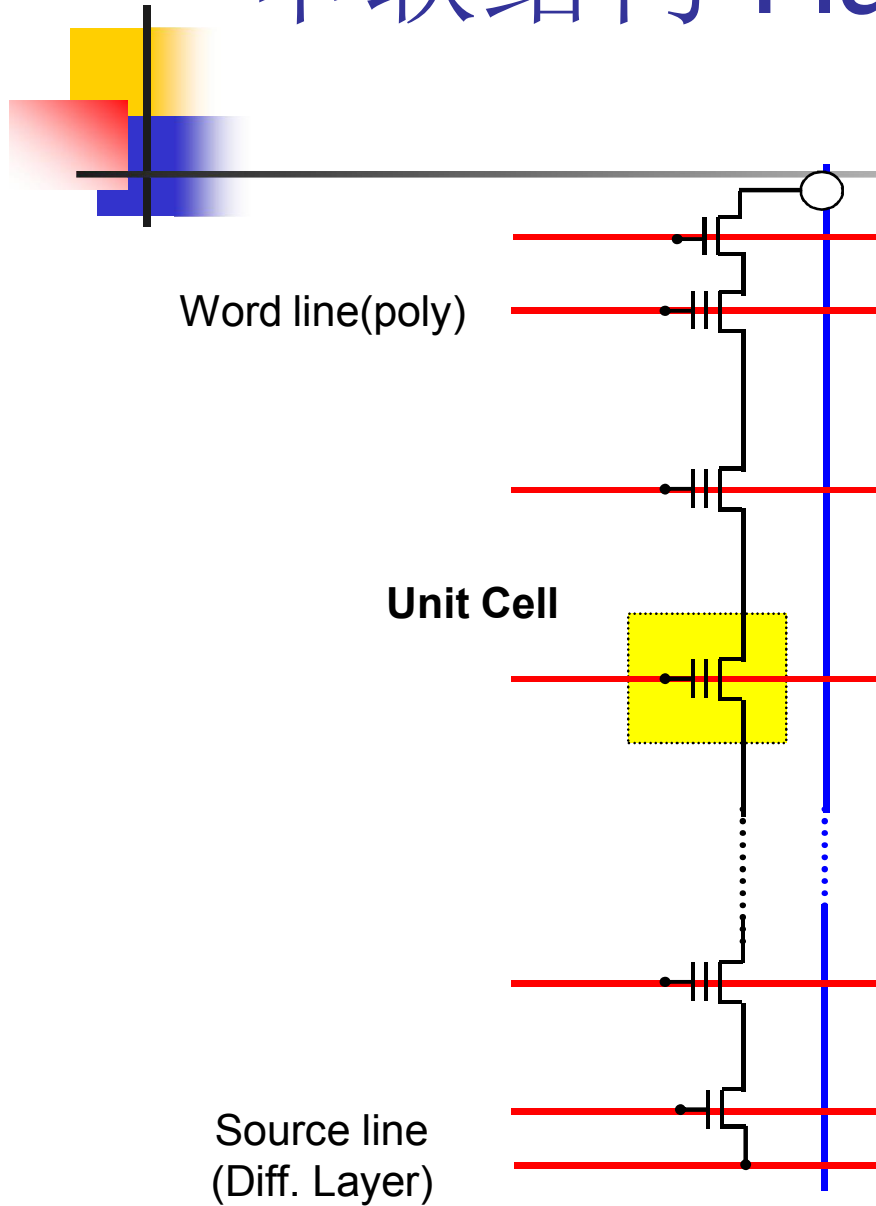

串联结构 Flash Memory

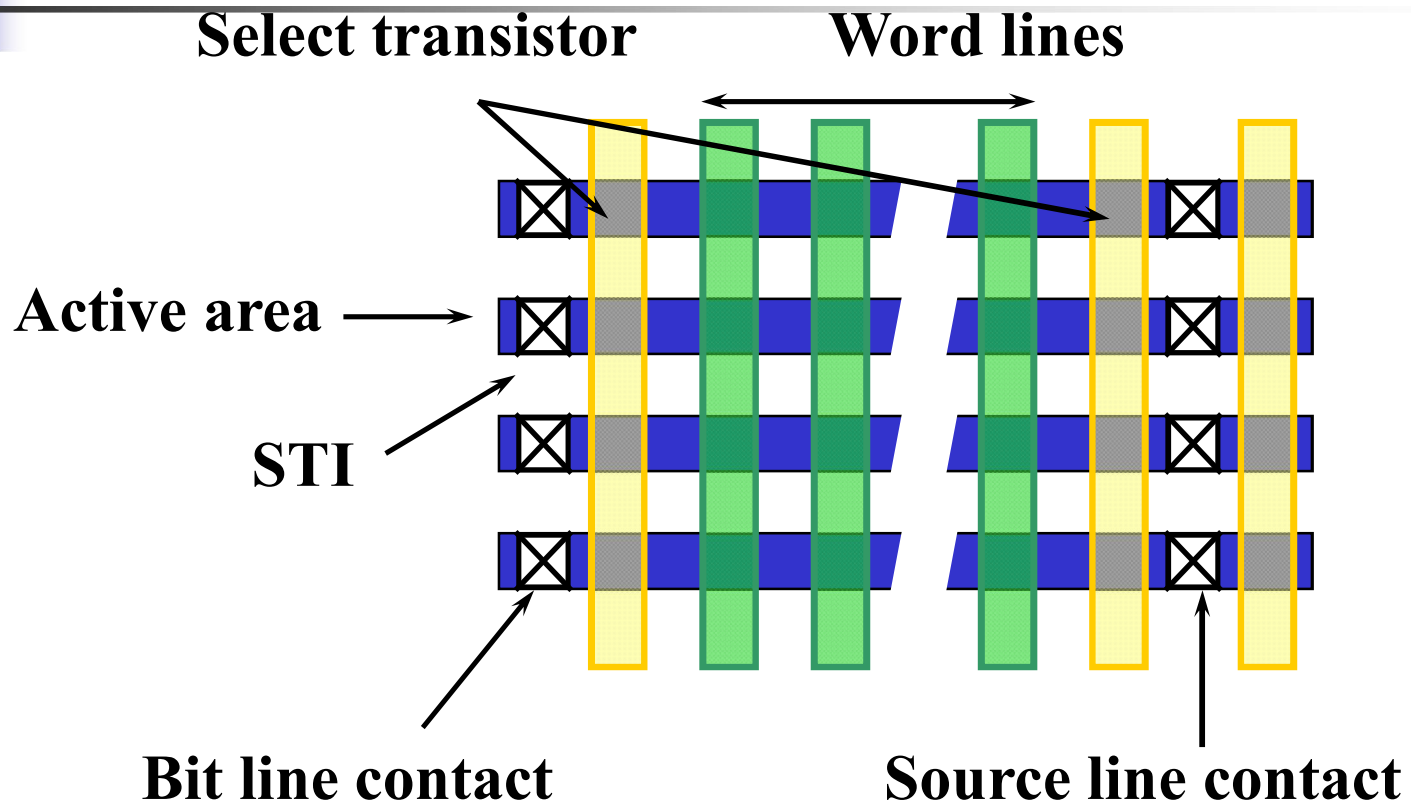

Courtesy Toshiba

Characteristics of ROM



Table 12-1 Comparison between nonvolatile memories ([Itoh01]).
 $V_{DD} = 3.3$ or 5 V; $V_{PP} = 12$ or 12.5 V.

	Cell— Nr. of Transistors	Cell Area (ratio wrt EPROM)	Mechanism		External Power Supply		Program/ Erase Cycles
			Erase	Write	Write	Read	
MASK ROM	1 T (NAND)	0.35–5	—	—	—	V_{DD}	0
EPROM	1 T	1	UV Exposure	Hot electrons	V_{PP}	V_{DD}	~100
EEPROM	2 T	3–5	FN Tunneling	FN Tunneling	V_{PP} (int)	V_{DD}	10^4 – 10^5
Flash Memory	1 T	1–2	FN Tunneling	Hot electrons	V_{PP}	V_{DD}	10^4 – 10^5
			FN Tunneling	FN Tunneling	V_{PP} (int)	V_{DD}	10^4 – 10^5